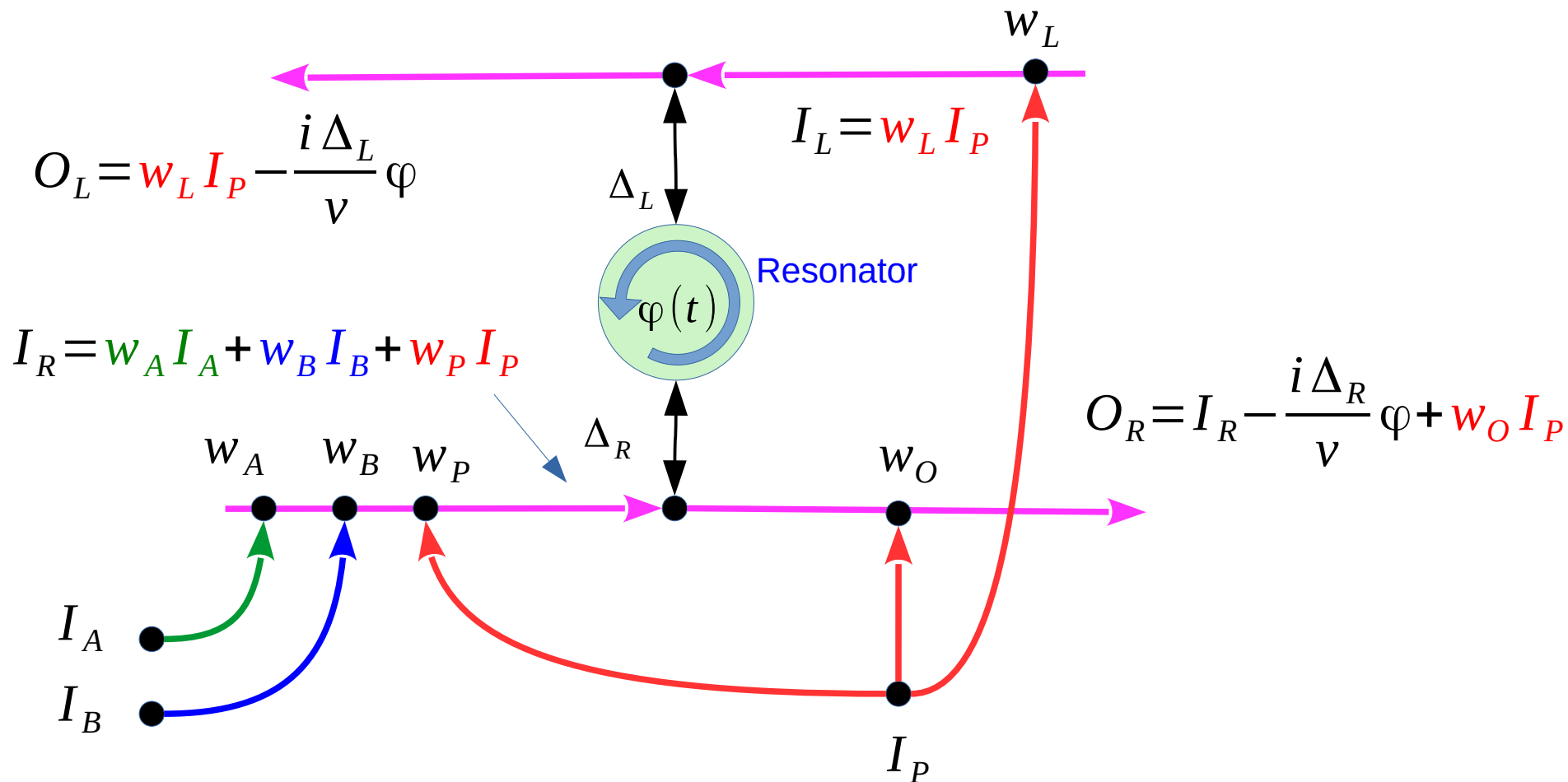


## Gate with a single resonator: circuitry



# Analytical model

Resonator inputs:

$$I_R = w_A I_A + w_B I_B + w_P I_P$$

$$I_L = w_L I_P$$

Logical

Power input (bias)

Outputs:

$$O_L = w_L I_P - \frac{i \Delta_L}{\nu} \varphi$$


Gate output  $\longrightarrow$   $O_R = I_R - \frac{i \Delta_R}{\nu} \varphi + w_O I_P$

Dynamics:  $\left( \omega - \Omega_0 + i \Gamma_{\text{tot}} - \lambda |\varphi|^2 \right) \varphi = \Delta_R^* I_R + \Delta_L^* I_L$   $\Gamma_{\text{tot}} \equiv \Gamma_0 + \frac{|\Delta_R|^2}{2\nu} + \frac{|\Delta_L|^2}{2\nu}$

Resonator params (real):  $\Omega_0, \Gamma_0, \lambda$       Hybridisation (complex):  $\Delta_R, \Delta_L$

Circuitry params (complex-valued!):  $w_A, w_B (=w_A), w_P, w_O, w_L$

## Case study: resonator

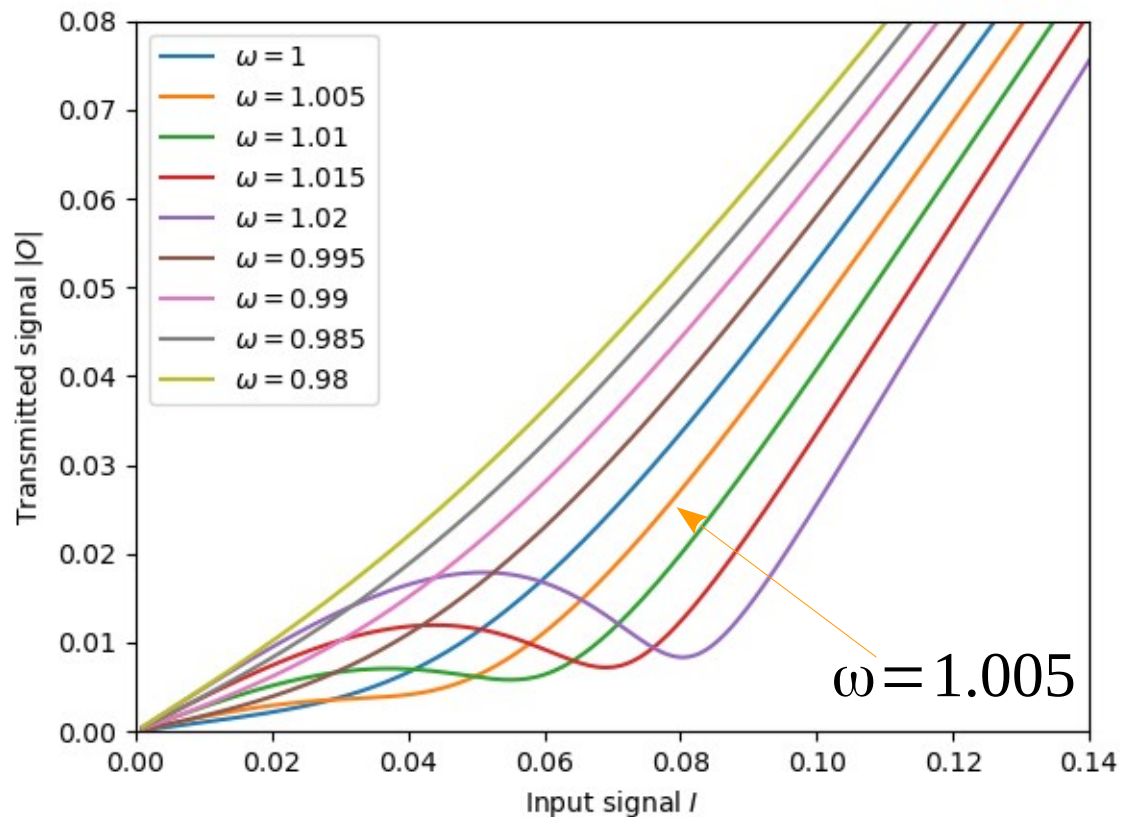

Resonator params:

$$\Omega_0 = 1.0 \quad \Gamma_0 = 0.005 \quad \lambda = 0.1$$

$$\nu = 1.0 \quad \Delta_R = 0.2 \quad \Delta_L = 0.15$$

$$\Gamma_R = 0.02 \quad \Gamma_L = 0.01125$$


$$\Gamma_{\text{tot}} = 0.03625$$

Characteristic scale  $I, O \sim 0.05$


Operating frequency  $\omega = 1.005$

# Case study: activation function


Amplitude response @ 1.005

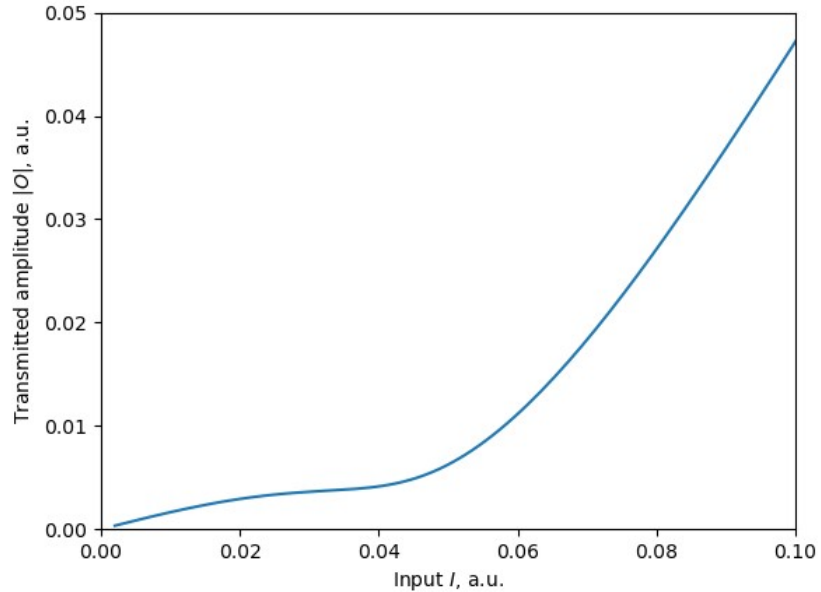

Phase @ 1.005

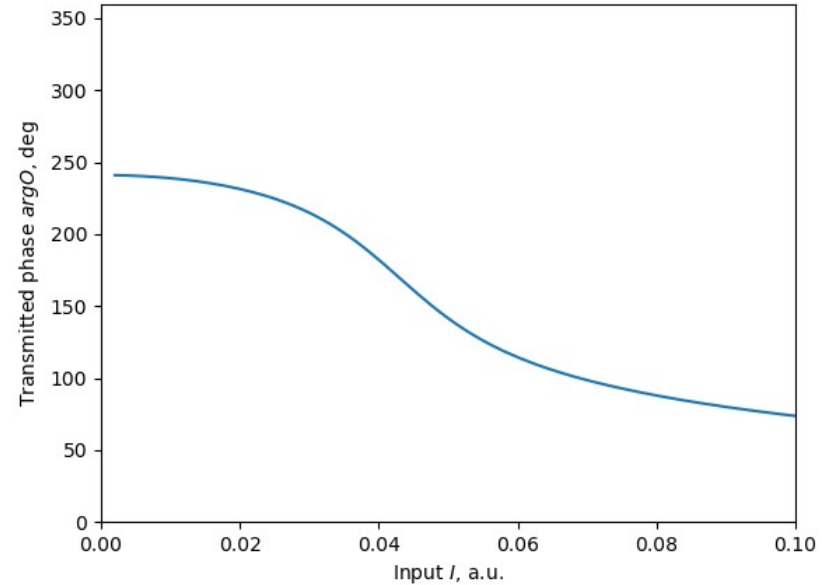

## Case study: Example output (analogue)

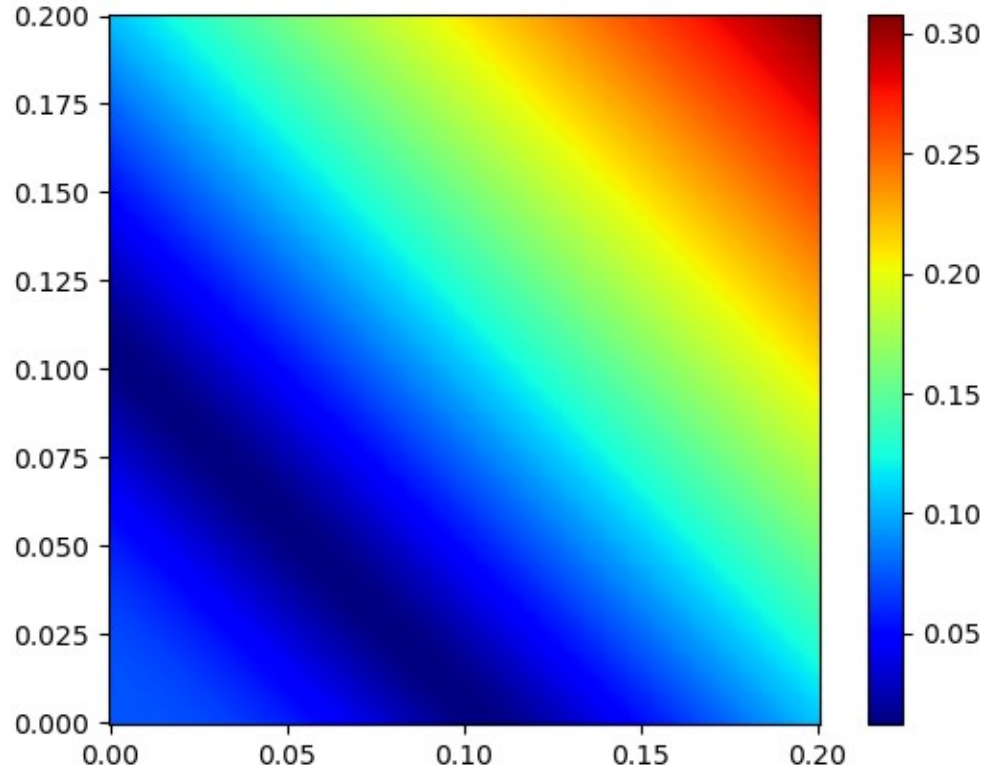

Circuitry:


$$w_A = w_B = 0.9 \quad w_P = 0.2$$

$$w_O = 0.5i \quad w_L = -0.5i$$

$$I_P = 0.08$$

NAND-like behaviour for  $I < 0.1$ ?

# Digital performance: fidelity as NAND

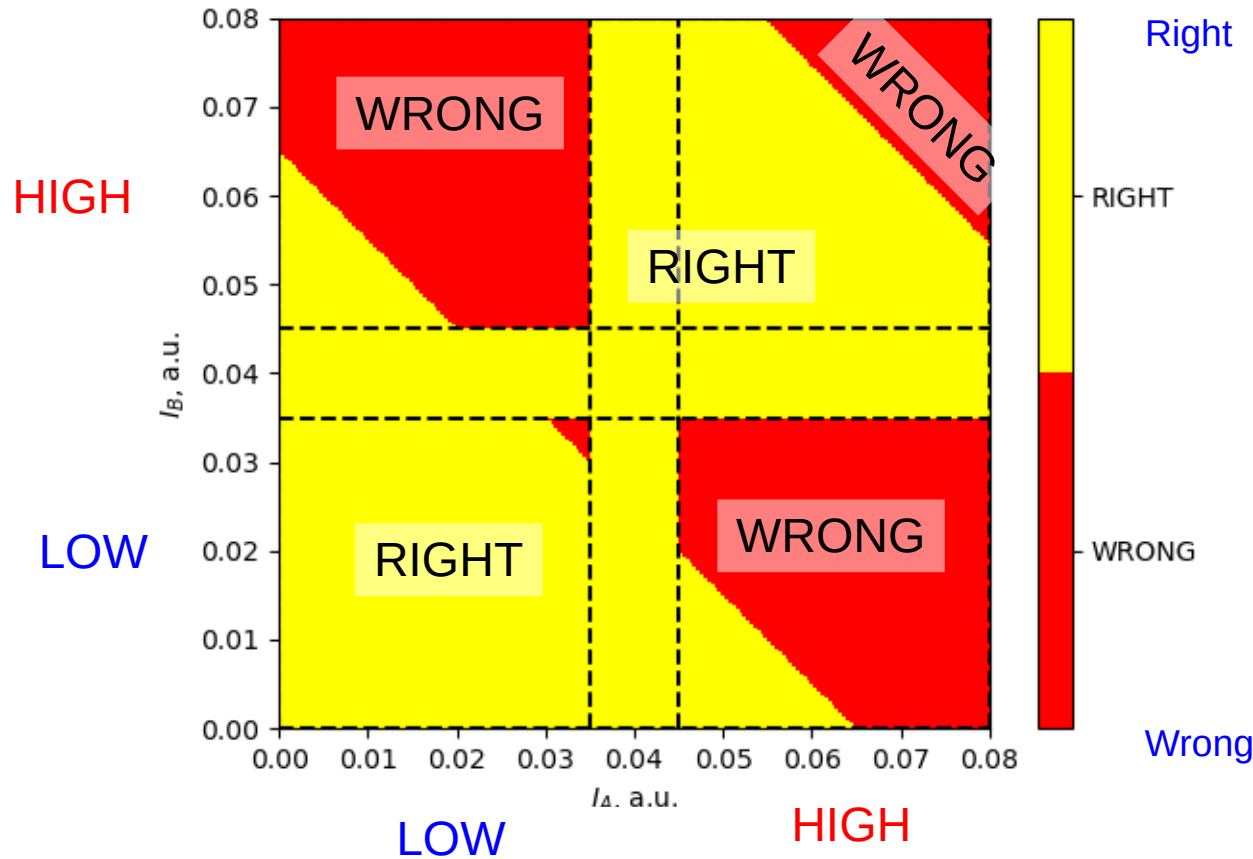


Logical levels:

$$0.0 < \text{LOW} < 0.035$$

$$0.045 < \text{HIGH} < 0.08$$

OTHERWISE: INVALID


Performance metric:  
Minimal WRONG area

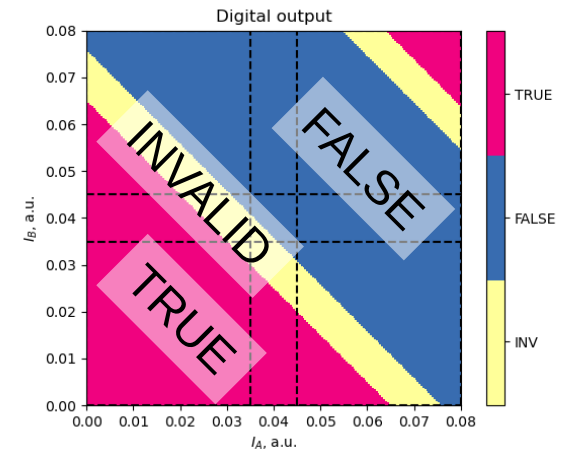
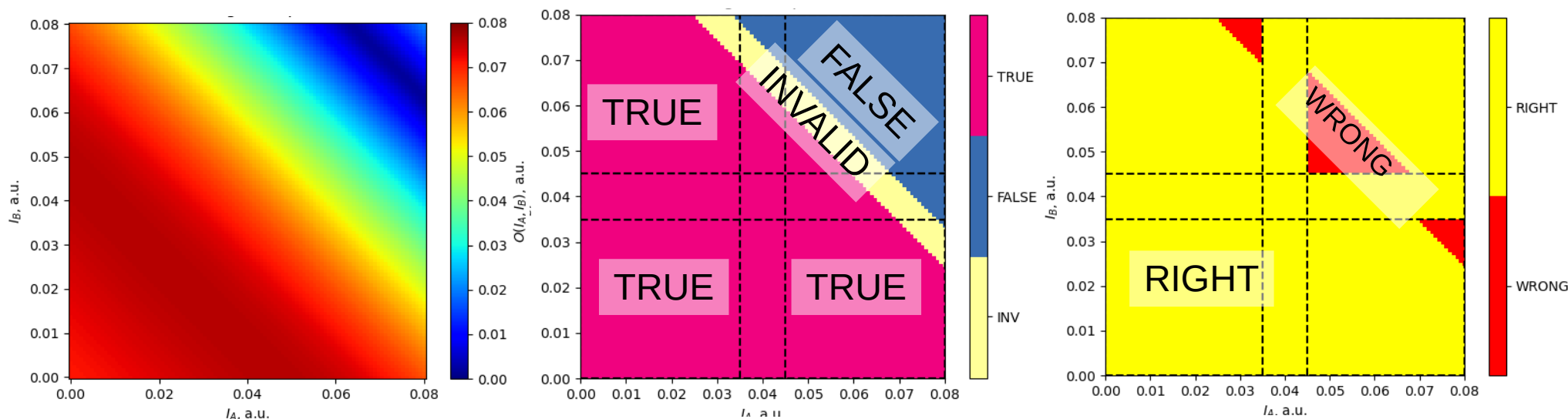
## Optimization (via differential evolution, with phases):

$$w_A = w_B = 0.977679, \quad w_P = -0.166609 - 0.112921i$$

$$w_L = -0.077261 + 0.360543i, \quad w_O = -0.362986 - 0.585067i$$



Obstacle: diagonality, dependence upon the linear combination  $w_A I_A + w_B I_B$

## Plan

- The weights on the gate (and other params) can be optimized
- Ditto operating frequency, etc

## Difficulties:

- “Diagonal” dependence:  $A + B$  enters trivially, poor approximation for logical gates
- Fidelity/score is not smooth (changes in steps), gradient-based algorithms are not directly applicable